

(Pages : 4)

L – 3939

Reg. No. : 33.220.95.9016

Name : Ashib Rehman: B

First Semester B.Sc./B.C.A. Degree Examination, August 2021

Career Related First Degree Programme Under CBCSS

Group 2(b) – Computer Science /Computer Applications

Complementary Course

CS 1131/CP1131 – DIGITAL ELECTRONICS

(2020-Admission Regular)

Time : 3 Hours

Max. Marks : 80

PART – A

Answer all questions. Each question carries 1 mark.

1. What is meant by peak inverse voltage?
2. Draw the V-I characteristics of Zener diode.
3. What is an emitter follower?
4. What do you mean by operating point?
5. Convert  $(101011.101)_2$  to decimal number.
6. Draw the truth table and logic symbol of NAND gate.
7. According to De-morgan's theorem,  $\overline{AB + CD}$  is equivalent to \_\_\_\_\_.
8. What do you mean by toggle condition?

P.T.O.

9. What are min terms?
10. How many flip flops are required to construct a decade counter?

(10 × 1 = 10 Marks)

PART – B

Answer **any eight** questions. Each question carries **2** marks.

11. Explain the V-I characteristics of PN junction diode.
12. What are the advantages of a bridge rectifier over a full wave centre tapped rectifier?
- ✓13. What are the three currents in a transistor and how they are related?
14. Why common collector circuit is called emitter follower?
- ✓15. Convert  $(255)_{10}$  to binary number.
- ✓16. Convert hexadecimal number 5B6 into decimal number.
- ✓17. Prove that  $A + \bar{A}. B + A.\bar{B} = A + B$ .
- ✓18. State De-Morgans theorems.
- ✓19. What is a quad in a Karnaugh map?
- ✓20. Draw the logic diagram of a half-adder.
21. Define multiplexer.
22. What are shift registers? List any two applications of shift register.
- ✓23. Differentiate SOP and POS.
24. Define Flip flop.



25. Draw the logic diagram of a 1-bit comparator.


26. What do you mean by decoder?

(8 × 2 = 16 Marks)

PART – C

Answer **any six** questions. Each question carries 4 marks.

- ✓ 27. What is a rectifier? Explain the working of a half wave rectifier with neat diagram.
28. Explain the operation of a transistor as an amplifier.
- ✓ 29. Convert the following to binary number
- (a)  $(125.625)_{10}$
  - (b)  $(615)_8$
  - (c)  $(10AF)_{16}$ .
- ✓ 30. Determine
- (a)  $10101 + 11001$
  - (b)  $1110 - 1011$ .
  - (c) 2's complement of 00111101.
- ✓ 31. Explain the rules of Boolean algebra.
- ✓ 32. Implement an OR function using NAND gates.
- ✓ 33. Differentiate min term and max term.
34. Explain the operation and truth table of J-K flip flop.
35. Differentiate synchronous and asynchronous counters.

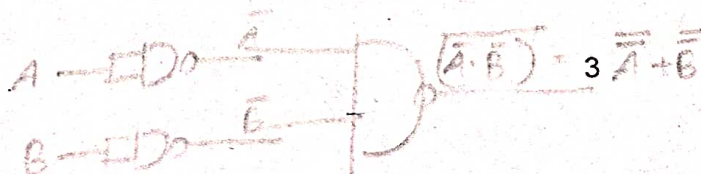

- ✓36. Explain the operation and logic circuit of full adder.
37. Explain the working of 2-bit comparator.
38. Differentiate multiplexer and decoder.

**(6 × 4 = 24 Marks)**

**PART – D**

Answer **any two** questions. Each question carries **15** marks.

39. With the help of diagram explain the working of a zener diode voltage regulator.
40. What is a multivibrator? Explain the working of astable multivibrator using 555 timer with neat circuit and waveforms.
41. What do you mean by NOR function? Explain the universal property of NOR gate.
- ✓42. Use K map to minimize  $f = \Sigma(0, 2, 3, 4, 6, 8, 10, 11, 12, 14)$
- ✓43. Explain in detail the operation and truth table of different type of flip flops.
44. Explain in detail the operation and logic circuit of different type of shift registers.

**(2 × 15 = 30 Marks)**